
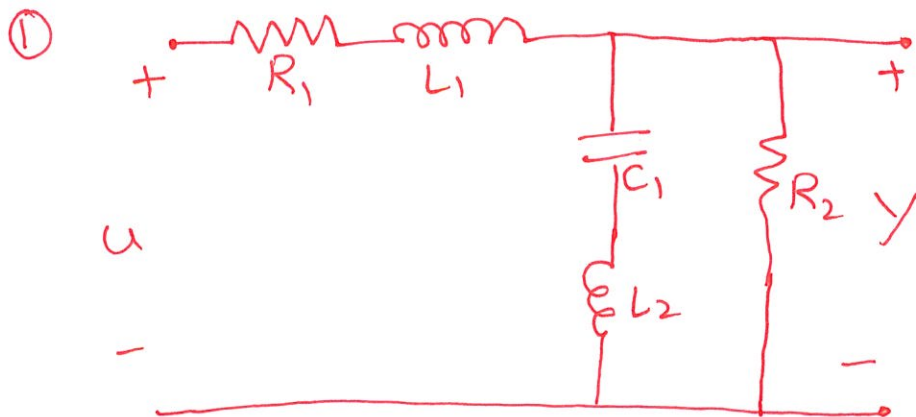


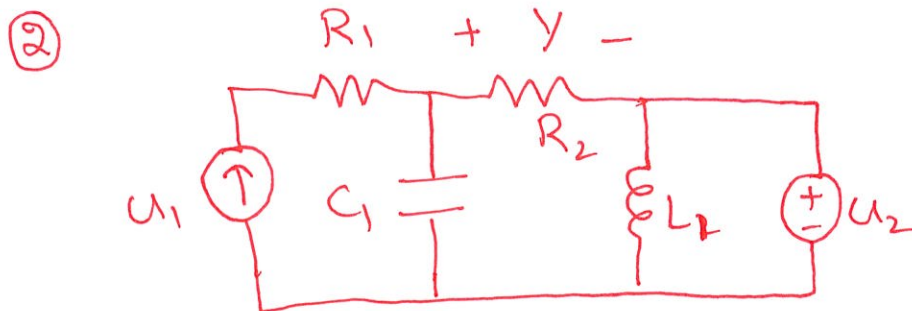
write the state & output equations for All 4 electrical ckts.




(2.5 Points)



(2.5 Points)

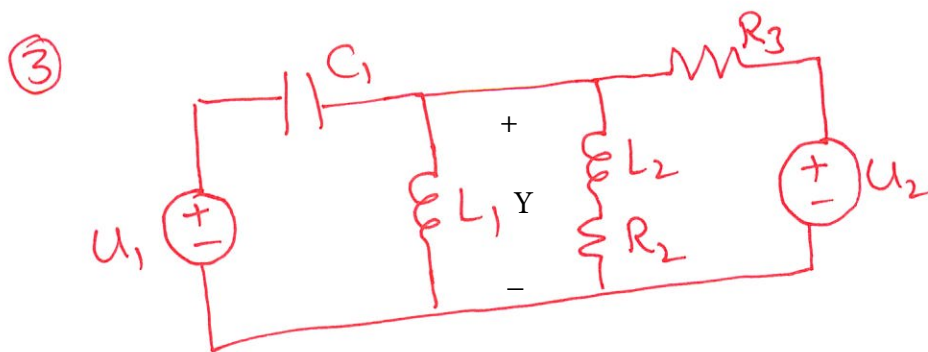

(2.5 Points)

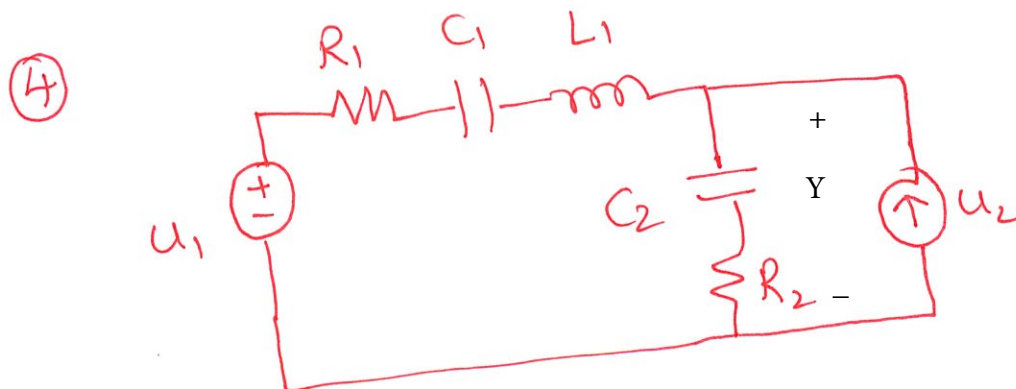

(2.5 Points)

$\begin{pmatrix} + \\ - \end{pmatrix} \Rightarrow$  Voltage source

$\begin{pmatrix} \uparrow \end{pmatrix} \Rightarrow$  Current source.